

Lab 4

TopIO_Interface

Interfaces with an FPGA. Here's a detailed explanation of its functionality:


Module Instantiations:

1. **Top Module:** The Top module is instantiated with its ports mapped to the relevant signals.
2. **Segment Decoders:** The segment decoders are instantiated to display values on the 7-segment displays:
 - DecoderModuleXHex0 and DecoderModuleXHex1 display the X vector.
 - DecoderModuleYHex2 and DecoderModuleYHex3 display the Y vector.
 - DecoderModuleOutHex4 and DecoderModuleOutHex5 display the ALUout vector.
3. **Clock Divider (PLL):** The pll_wrap module divides the input clock by 2^L , where L is set to 6.

The code:

- Manages inputs from switches and keys.
- Displays processed data on 7-segment displays.
- Controls LEDs based on ALU flags.
- Outputs a PWM signal.
- Includes a clock divider for internal timing.

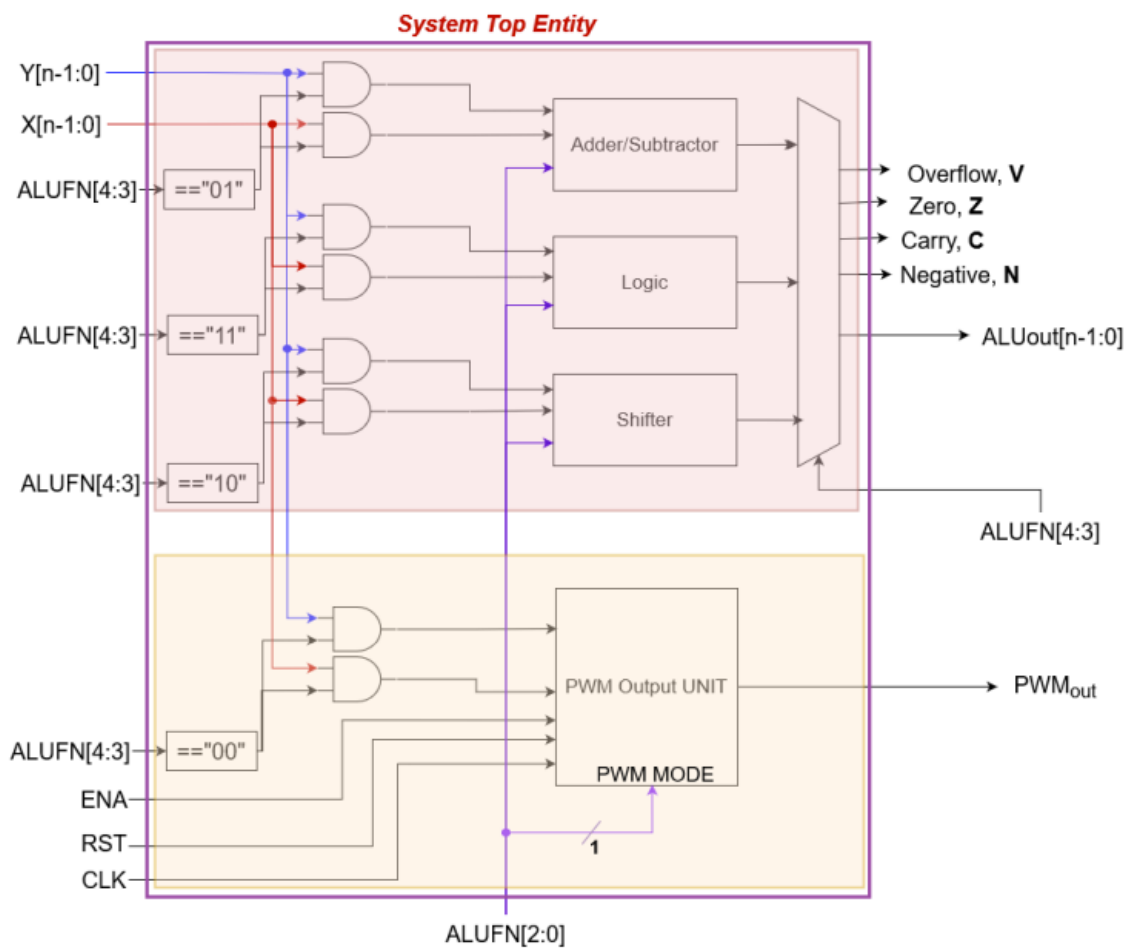In essence, the top module orchestrates the interaction between the PWM generation and the ALU operations, handling the inputs and outputs efficiently through these two instantiated components.



PWM

The PWM module generates a Pulse Width Modulation (PWM) signal based on input control signals and vectors. Here is a high-level description of what it does and how it works logically:

Functionality

The module generates a PWM signal where the duty cycle is determined by comparing a counter with input thresholds. The behavior is controlled by the $ALUFN$ input.

Logical Operation

Initialization:

- When the reset (RST) signal is high, the counter (COUNTER_PWM) and the PWM output register (PWM_OUT_REG) are reset to zero.

Clock Process:

- On the rising edge of the clock (CLK), if the enable signal (ENA) is high and the most significant bits of ALUFN are "00", the PWM generation logic is active.

Counter Increment:

- The counter increments on each clock cycle. If the counter reaches the value of Y_PWM, it resets to zero, creating a repetitive counting cycle.

PWM Signal Generation:

- The PWM output register (PWM_OUT_REG) is set based on the counter value and the values of X_PWM and Y_PWM:
 - If ALUFN is "00000", the PWM signal is high when the counter is between X_PWM and Y_PWM.
 - If ALUFN is "00001", the PWM signal is low when the counter is between X_PWM and Y_PWM, and high otherwise.

 


Figure 2 RTL of PWM

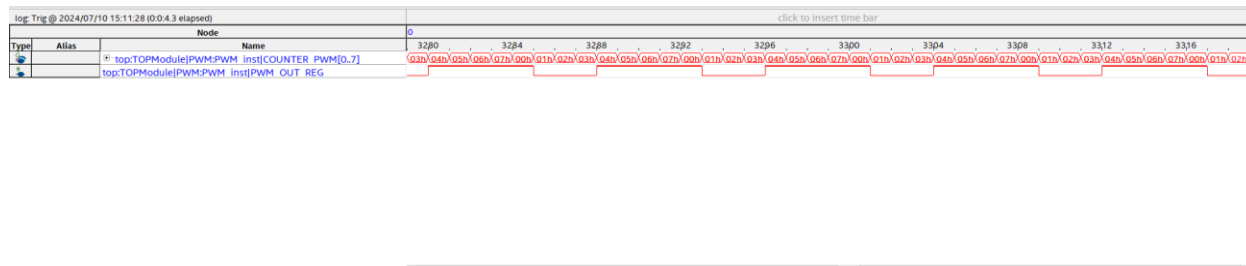


Figure 3 - Wave form in Quartus

Compilation Report - PWM_timing_analysis X			
Slow 1100mV 85C Model Fmax Summary			
<<Filter>>			
	Fmax	Restricted Fmax	Clock Name
1	371.2 MHz	371.2 MHz	CLK

Figure 4 - max freq

ALU

The ALU module in VHDL performs arithmetic, logical, and shifting operations based on the input control signals. Here is a high-level description of what it does and how it works logically:

Functionality

The module computes the result of various operations (addition/subtraction, logical operations, and shifts) based on the ALUFN_i control signal. It then outputs the result along with several status flags.

Logical Operation

1. Component Instantiation:

- **AdderSub Component:** Handles addition and subtraction operations.
- **Shifter Component:** Handles bitwise shift operations.
- **Logic Component:** Handles logical operations (AND, OR, etc.).

2. Input Gating:

- Inputs to the specific components (AdderSub, Shifter, Logic) are gated based on the most significant bits of ALUFN_i:
 - 01 for AdderSub
 - 10 for Shifter
 - 11 for Logic

3. Overflow Detection:

- Overflow (Vflag) is calculated for addition and subtraction based on specific conditions:

- **Addition Overflow (Vflag_add):** Occurs when adding two positive numbers results in a negative or adding two negative numbers results in a positive.
- **Subtraction Overflow (Vflag_sub):** Occurs when subtracting a positive number from a negative results in a positive or subtracting a negative number from a positive results in a negative.

4. Output Logic:

- The result from the appropriate component is selected based on ALUFN_i and assigned to ALUOUT.
- The status flags are calculated based on the result and the ALUFN_i:
 - **Zero Flag (Zflag_o):** Set if the result is zero.
 - **Negative Flag (Nflag_o):** Set if the most significant bit of the result is 1.
 - **Carry Flag (Cflag_o):** Set based on the carry out from the AdderSub or Shifter components.

5. Output Assignment:

- The final result is assigned to ALUout_o.

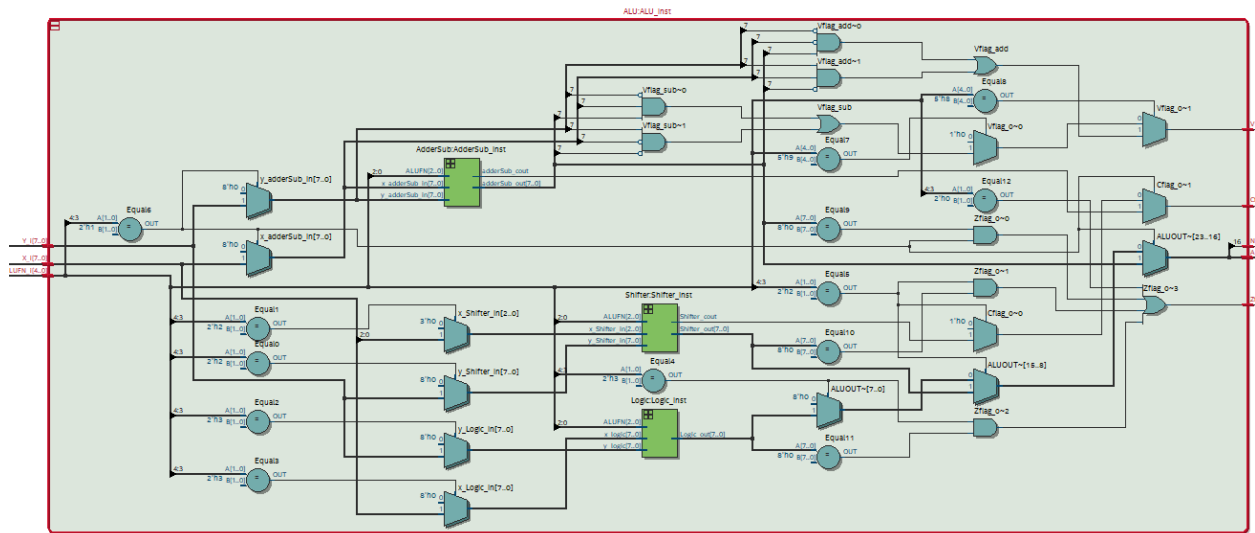


Figure 5 -RTL of ALU

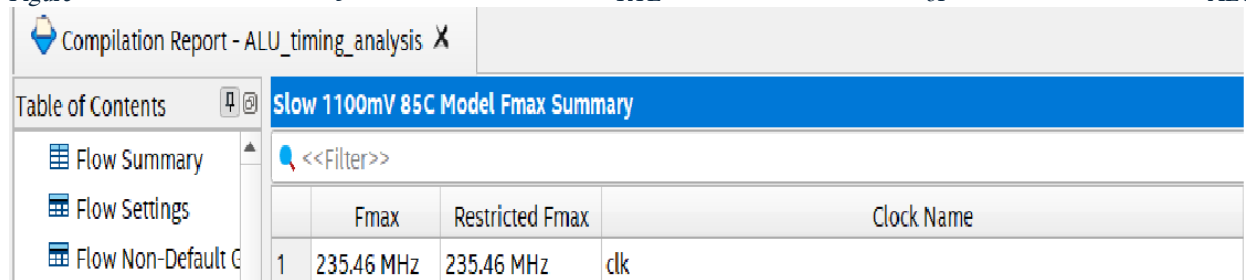
 


Figure 6 - max freq of alu

TB

Figure 7 - *alu* *logic*

[illegible]

Critical path

